

1. (a) A shunt LC resonator comprising L_n and C_n is to be compared with a quarter-wavelength short-circuited stub of characteristic impedance Z_{0n} .
- Determine the admittance of the shunt LC resonator at angular frequencies near the resonance frequency, i.e., $\omega \approx \omega_0$, where $\omega_0^2 = 1/(L_n C_n)$.
 - Determine the admittance of the short-circuited stub at angular frequencies $\omega \approx \omega_0$, where ω_0 corresponds to 90° phase shift.
 - Using suitable approximations of your answers above, find the expression of Z_{0n} in terms of L_n and C_n .


1. (a) 一个由 L_n 和 C_n 并联组成的 LC 谐振器，与一个特性阻抗为 Z_{0n} 的 $1/4$ 波长短路支节相比较

(i) 计算该 LC 并联谐振器在接近谐振频率时的导纳 ($\omega \approx \omega_0$ $\omega_0 = \frac{1}{\sqrt{L_n C_n}}$)

(ii) 计算该短路支节在接近共振频率时的导纳 ($\omega \approx \omega_0$ ω_0 对应 90° 相移)

(iii) 在上述计算的基础上，找出 Z_{0n} 用 C_n 和 L_n 如何表示。

解题思路: (i)

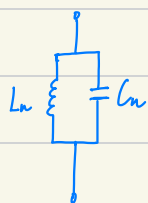

$$Y_L = \frac{1}{j\omega L_n}$$

$$Y_C = j\omega C_n$$

$$Y = Y_L + Y_C = \frac{1}{j\omega L_n} + j\omega C_n$$

$$\text{当工作在谐振频率上时 } \omega \approx \omega_0 = \frac{1}{\sqrt{L_n C_n}} + \Delta\omega$$


$$Y = \frac{1}{j\omega_0 L_n} + j\omega_0 C_n = \frac{1}{j(\frac{1}{\sqrt{L_n C_n}} + \Delta\omega) L_n} + j(\frac{1}{\sqrt{L_n C_n}} + \Delta\omega) C_n$$

$$= \frac{1}{j(1 + \frac{\Delta\omega}{\omega_0}) \omega_0 L_n} + j(1 + \frac{\Delta\omega}{\omega_0}) \omega_0 C_n = j\omega_0 C_n \left[1 + \frac{\Delta\omega}{\omega_0} - \frac{1}{1 + \frac{\Delta\omega}{\omega_0}} \right] = j\omega_0 C_n \frac{(\frac{\Delta\omega}{\omega_0})^2 + 2\frac{\Delta\omega}{\omega_0}}{1 + \frac{\Delta\omega}{\omega_0}}$$

$$= \frac{\sqrt{L_n C_n}}{j(1 + \frac{\Delta\omega}{\omega_0}) L_n} + j \frac{\sqrt{C_n}}{\sqrt{L_n}} + j\Delta\omega \cdot C_n = -j \sqrt{\frac{C_n}{L_n}} \cdot \frac{1}{1 + \frac{\Delta\omega}{\omega_0}} + j \sqrt{\frac{C_n}{L_n}} + j \frac{\Delta\omega}{\omega_0} \cdot \sqrt{\frac{C_n}{L_n}}$$

$$= j \sqrt{\frac{C_n}{L_n}} \left[1 + \frac{\Delta\omega}{\omega_0} - \frac{1}{1 + \frac{\Delta\omega}{\omega_0}} \right] = j \sqrt{\frac{C_n}{L_n}} \frac{(1 + \frac{\Delta\omega}{\omega_0})^2 - 1}{1 + \frac{\Delta\omega}{\omega_0}} = j \sqrt{\frac{C_n}{L_n}} \frac{(\frac{\Delta\omega}{\omega_0})^2 + 2\frac{\Delta\omega}{\omega_0}}{1 + \frac{\Delta\omega}{\omega_0}}$$
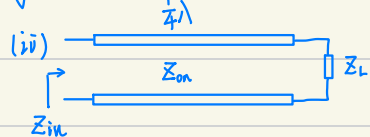
$$= j \sqrt{\frac{C_n}{L_n}} \frac{\Delta\omega^2 + 2\omega_0 \Delta\omega}{\omega_0^2 + \omega_0 \Delta\omega} \quad \star$$



$$Z_{in} = Z_0 \cdot \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

$$\therefore Z_0 = Z_{0n} \quad Z_L = 0$$

$$\therefore Z_{in} = Z_{0n} \cdot \frac{jZ_{0n} \tan \beta l}{Z_{0n}}$$

$$= jZ_{0n} \cdot \tan \left(\frac{\pi C}{2\omega_0} \cdot \frac{\omega_0 + \Delta\omega}{c} \right) = jZ_{0n} \tan \left[\frac{\pi}{2} \cdot \left(1 + \frac{\Delta\omega}{\omega_0} \right) \right]$$

$$\beta = \frac{2\pi}{\lambda'} \quad l = \frac{\lambda}{4} \quad \omega = \omega_0 + \Delta\omega$$

$$\lambda = \frac{c}{\omega_0/2\pi} \quad \lambda' = \frac{c}{(\omega_0 + \Delta\omega)/2\pi}$$

$$\beta = \frac{2\pi}{\frac{c \cdot 2\pi}{\omega_0 + \Delta\omega}} = \frac{\omega_0 + \Delta\omega}{c}$$

$$l = \frac{2\pi C}{4\omega_0} = \frac{\pi \cdot C}{2\omega_0}$$

$$\tan(A+B) = \frac{\tan A + \tan B}{1 - \tan A \tan B} \quad \text{原式} = j \cdot Z_{0n} \cdot \frac{\tan \frac{\pi}{2} + \tan \frac{\pi}{2} \cdot \frac{\Delta\omega}{\omega_0}}{1 - \tan \frac{\pi}{2} \cdot \tan \frac{\pi}{2} \cdot \frac{\Delta\omega}{\omega_0}} = j \cdot Z_{0n} \cdot (-\cot \frac{\pi}{2} \frac{\Delta\omega}{\omega_0}) = -j Z_{0n} \cdot \cot \left(\frac{\pi}{2} \frac{\Delta\omega}{\omega_0} \right)$$


$$\therefore Y_{in} = 1/Z_{in} = j \frac{1}{Z_{0n}} \cdot \tan \left(\frac{\pi}{2} \frac{\Delta\omega}{\omega_0} \right) \quad \star$$

$$(iii) \text{ 若 } Y_{in} = Y, \text{ 则 } j \frac{1}{Z_{0n}} \tan \left(\frac{\pi \Delta\omega}{2\omega_0} \right) = j \sqrt{\frac{C_n}{L_n}} \frac{\Delta\omega^2 + 2\omega_0 \Delta\omega}{\omega_0^2 + \omega_0 \Delta\omega}$$

$$\therefore Z_{0n} = \lim_{\Delta\omega \rightarrow 0} \sqrt{\frac{L_n}{C_n}} \cdot \frac{\tan \frac{\pi}{2} \frac{\Delta\omega}{\omega_0}}{\frac{\Delta\omega^2 + 2\omega_0 \Delta\omega}{\omega_0^2 + \omega_0 \Delta\omega}} = \sqrt{\frac{L_n}{C_n}} \cdot \lim_{\Delta\omega \rightarrow 0} \frac{\frac{\pi}{2} \frac{\Delta\omega}{\omega_0} \cdot \omega_0^2}{\Delta\omega^2 + 2\omega_0 \Delta\omega} = \sqrt{\frac{L_n}{C_n}} \cdot \frac{\pi}{2} \cdot \omega_0 \cdot \lim_{\Delta\omega \rightarrow 0} \frac{\Delta\omega}{\Delta\omega^2 + 2\omega_0 \Delta\omega}$$

$$Z_{0n} = \frac{\pi}{4} \sqrt{\frac{L_n}{C_n}} \quad \star$$
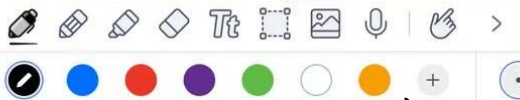
$$= \sqrt{\frac{L_n}{C_n}} \cdot \frac{\pi}{2} \cdot \omega_0 \cdot \frac{1}{2\omega_0} = \frac{\pi}{4} \sqrt{\frac{L_n}{C_n}}$$




$$\lim_{\Delta\omega \rightarrow 0} \frac{j\sqrt{L_n} \frac{\Delta\omega^2 + 2\Delta\omega \cdot \omega_0}{\omega_0^2 + \Delta\omega \cdot \omega_0}}{j2\Delta\omega \cdot L_n}$$

$$f(x) = f(x_0) + \frac{f'(x_0)}{1!} (x - x_0) + \frac{f''(x_0)}{2!} (x - x_0)^2 + \dots$$

$$\frac{1}{\omega_0 + \Delta\omega} = \frac{1}{\omega_0} - \frac{\Delta\omega}{\omega_0^2}$$

$$\left(\frac{1}{\omega}\right)' = -\frac{1}{\omega^2}$$

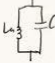(i) 

$$Y_{LC} = j\omega L_n + \frac{1}{j\omega C_n}$$

$$\omega \approx \omega_0$$

$$\omega = \omega_0 + \Delta\omega \quad \omega^2 = \frac{1}{L_n C_n}$$

$$Y_{in} = j(\omega_0 + \Delta\omega)C_n + \frac{1}{j(\omega_0 + \Delta\omega)L_n}$$

$$= j[(\omega_0 + \Delta\omega)C_n - \frac{1}{\omega_0 L_n} + \frac{\Delta\omega}{\omega_0^2 L_n}]$$

$$= j2\Delta\omega C_n$$


$$= \frac{1}{2L_n\sqrt{C_n}} \lim_{\Delta\omega \rightarrow 0} \frac{\Delta\omega^2 + 2\Delta\omega \cdot \omega_0}{\Delta\omega(\omega_0 + \omega_0)} = \frac{1}{L_n\sqrt{C_n}} \cdot \frac{1}{j\sqrt{L_n C_n}} = \frac{1}{\omega_0^2}$$

$$\omega_0^2 = \frac{1}{L_n C_n} = \frac{1}{C_n} \sqrt{\frac{C_n}{L_n}} \cdot \frac{1}{j\sqrt{L_n C_n}} = \frac{1}{\omega_0^2}$$

$$\omega_0 L_n = \frac{1}{\omega_0 C_n}$$

$$j[(\omega_0 + \Delta\omega)C_n - \omega_0 C_n + \omega_0 C_n \cdot \frac{\Delta\omega}{\omega_0}]$$


$$= j2\Delta\omega C_n$$

(ii) 

$$\tan\left(\frac{\pi}{2} + \phi\right) = \frac{\sin\left(\frac{\pi}{2} + \phi\right)}{\cos\left(\frac{\pi}{2} + \phi\right)}$$

$$= \frac{\sin\frac{\pi}{2}\cos\phi + \cos\frac{\pi}{2}\sin\phi}{\cos\frac{\pi}{2}\cos\phi - \sin\frac{\pi}{2}\sin\phi}$$

$$= \frac{\cos\phi}{-\sin\phi} = -\frac{1}{\tan\phi} \approx -\frac{1}{\phi}$$

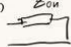(ii) 

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\phi)}{Z_0 + jZ_L \tan(\phi)}$$

$$Z_L = 0$$

$$Z_{in} = jZ_0 \tan(\phi)$$

$$Y_{in} = \frac{1}{Z_{in}} = \frac{1}{jZ_0 \tan(\phi)} = \frac{1}{jZ_0 \cdot \left(-\frac{1}{\phi}\right)} = \frac{j\phi}{Z_0}$$

$$\Delta\phi = \frac{\Delta\omega}{\omega_0} \quad \phi_p = \frac{2\pi}{\omega_0} \Delta\omega \quad \Delta\phi = \frac{\Delta\omega \omega_0}{2\pi \omega_0} \cdot \frac{\pi}{4} = \frac{\Delta\omega \omega_0}{8\pi}$$

$$Y_{in} = \frac{j\Delta\omega \cdot \omega_0}{Z_0 \cdot 8\pi}$$

(iii)

$$(8\pi Z_0) j2\Delta\omega C_n = j\Delta\omega \cdot \omega_0$$

$$\frac{1}{\sqrt{L_n C_n}} \cdot \frac{1}{16\pi C_n}$$


$$Z_0 = \frac{1}{16\pi C_n} = \frac{1}{16\pi C_n L_n \omega_0^2} \cdot \sqrt{L_n C_n}$$

- (b) Based on the quarter-wavelength short-circuited stubs and transmission line sections, design a fifth-order bandpass filter with 0.5 dB equal ripple response. The center frequency is 2 GHz, the fractional bandwidth is 0.2 and the impedance is 50Ω . Using a table, list down the low-pass prototype values and the stub characteristic impedances. Sketch the schematic of the designed filter and highlight any potential issue with its microstrip implementation.

Answer: $N=5$ $\alpha_{\max}=0.5 \text{ dB}$ Chebyshev bandpass filter $f_0=2 \text{ GHz}$ $\Delta=0.2$
 $Z_0=50 \Omega$

5 1.7058 1.2296 2.5408 1.2296 1.7058 1.0000

| n | g_n | Z_{0n} |
|-----|--------|----------|
| 1 | 1.7058 | 4.6043 |
| 2 | 1.2296 | 6.3874 |
| 3 | 2.5408 | 3.0911 |
| 4 | 1.2296 | 6.3874 |
| 5 | 1.7058 | 4.6043 |
| 6 | 1.0000 | |

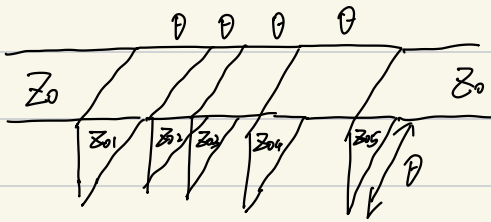

$$Z_{0n} = \frac{\pi Z_0 \Delta}{4 g_n}$$

2. A microwave transistor has the following S parameters at 1 GHz in a 50-Ω system:

$$S_{11} = 0.5 \angle 180^\circ$$

$$S_{12} = 0.08 \angle 30^\circ$$

$$S_{21} = 2.5 \angle 70^\circ$$

$$S_{22} = 0.8 \angle -100^\circ.$$

- (a) Check if the transistor is unconditionally stable using single-parameter stability criterion. Without using stability circles, discuss if it is stable to operate with the source and load reflection coefficients given by $\Gamma_s = 0.5 \angle 180^\circ$ and $\Gamma_L = 0.1 \angle 90^\circ$ respectively.

Answer: $\Delta = S_{11} \cdot S_{22} \cdot S_{12} \cdot S_{21} = 0.2228 \angle 62.12^\circ$

$$|\Delta| = 0.2228 < 1$$

$$K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2|S_{12} S_{21}|} \approx 0.399 < 1$$

The transistor is not unconditionally stable

$$K_t = \frac{3 - 2|S_{11}|^2 - 2|S_{22}|^2 + |\Delta|^2 - |1 - |\Delta|^2|}{4|S_{12} S_{21}|} > 1$$

$$K_t = 0.399 < 1$$

$$C_1 = S_{11} - S_{22}^* \Delta$$

$$C_2 = S_{22} - S_{11}^* \Delta$$

$$C_1 = 0.65 \angle -170.31^\circ$$

$$C_2 = 0.69 \angle -97.18^\circ$$

$$c_s = \frac{C_1^*}{|S_{11}|^2 - |\Delta|^2}$$

$$r_s = \frac{|S_{12} S_{21}|}{||S_{11}|^2 - |\Delta|^2|}$$

$$c_L = \frac{C_2^*}{|S_{22}|^2 - |\Delta|^2}$$

$$r_L = \frac{|S_{12} S_{21}|}{||S_{22}|^2 - |\Delta|^2|}$$

$$C_s = 3.24 \angle 170.31^\circ$$

$$r_s = 0.9982$$

$$C_L = 1.169 \angle 97.18^\circ$$

$$r_L = 0.3388$$

When $\Gamma_s = 0.5 \angle 180^\circ$ / $\Gamma_L = 0.1 \angle 90^\circ$, the network is stable

- (b) Using the above source and load reflection coefficients, calculate the resultant transducer power gain in dB. Design the input and output matching networks using quarter-wavelength transformers.

Answer : $\Gamma_s = 0.5 \angle 180^\circ$ $\Gamma_L = 0.1 \angle 90^\circ$

$$\Gamma_{in} = \frac{S_{11} - \Delta \Gamma_L}{1 - S_{22} \Gamma_L} = 0.5214 \angle -177.62^\circ$$

$$\Gamma_{out} = \frac{S_{22} - \Delta \Gamma_s}{1 - S_{11} \Gamma_s} = 0.9264 \angle -97.18^\circ$$

$$G_t = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_{in} \Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

$$G_t = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out} \Gamma_L|^2}$$

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} = \frac{S_{11} - \Delta \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s} = \frac{S_{22} - \Delta \Gamma_s}{1 - S_{11} \Gamma_s}$$

$$\Delta = S_{11} S_{22} - S_{12} S_{21}$$

3. (a) A four-port directional coupler is characterized by the following S parameters:

$$[S] = \begin{bmatrix} 0.02 & 0.8 & j0.5 & j0.03 \\ 0.8 & 0.02 & j0.03 & j0.5 \\ j0.5 & j0.03 & 0.02 & 0.8 \\ j0.03 & j0.5 & 0.8 & 0.02 \end{bmatrix}$$

Assuming the input is at port 1, calculate the return loss, coupling, isolation and directivity in dB. Give the relation among these quantities if any.

(10 Marks)

$$C = 10 \log_{10} \frac{P_1}{P_3} = -20 \log_{10} |S_{13}| \approx 6.02 \text{ dB} \quad I = C + D$$

$$I = 10 \log_{10} \frac{P_1}{P_4} = -20 \log_{10} |S_{14}| \approx 30.46 \text{ dB}$$

$$D = 10 \log_{10} \frac{|P_3|}{|P_4|} = -20 \log_{10} \frac{|S_{14}|}{|S_{13}|} \approx 24.44 \text{ dB}$$

$$RL = -20 \log_{10} |S_{11}| \approx 33.98$$