
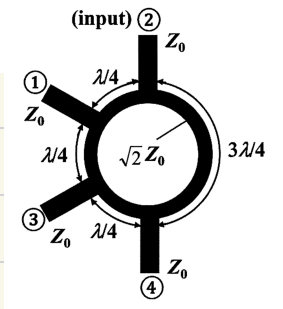


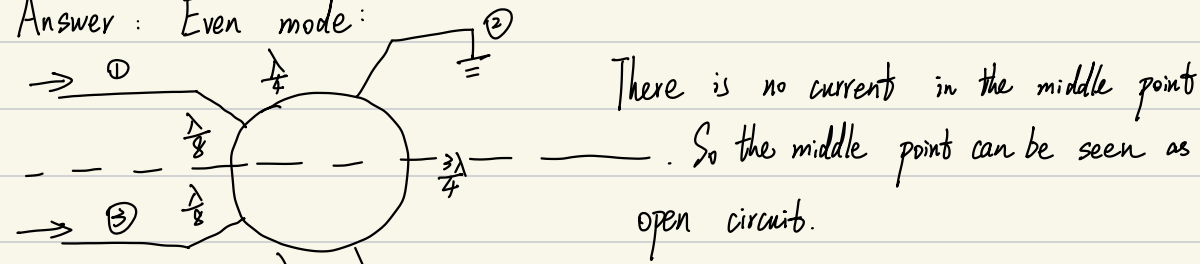1. (a) Figure 1 on page 2 shows a four-port hybrid ring coupler circuit with the input at port 2. With the aid of even- and odd-mode bisections of the circuit, derive the even- and odd-mode ABCD and S parameters ($S_{12,e}, S_{22,e}, S_{12,o}, S_{22,o}$).




Answer: Even mode:



$$[ABCD]_{\text{even}} = \begin{bmatrix} 1 & 0 \\ j\frac{Y_0}{2} & 1 \end{bmatrix} \begin{bmatrix} 0 & j\sqrt{2}Z_0 \\ j\frac{Y_0}{2} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -j\frac{Y_0}{2} & 1 \end{bmatrix}$$

$$= \begin{pmatrix} 0 & j\sqrt{2}Z_0 \\ j\frac{Y_0}{2} & -1 \end{pmatrix} \begin{pmatrix} 1 & 0 \\ -j\frac{Y_0}{2} & 1 \end{pmatrix}$$
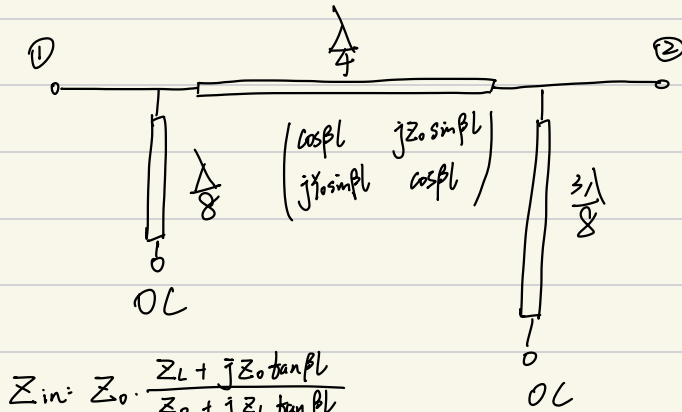
$$= \begin{pmatrix} 1 & j\sqrt{2}Z_0 \\ j\sqrt{2}Y_0 & -1 \end{pmatrix}$$



$$Z_{in} = Z_0 \cdot \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$


开路: $Z_L = \infty$

$$Z_{in} = Z_0 \cdot \frac{1}{j \tan \beta l}$$

$$S_{12e} = \frac{2(AD - BC)}{A + B/Z_0 + C Z_0 + D} = \frac{2(-1 - 2)}{1 + j\sqrt{2} + j\sqrt{2} - 1} = \frac{-6}{j2\sqrt{2}} = j\frac{3\sqrt{2}}{2}$$

$$S_{22e} = \frac{-A + B/Z_0 - C Z_0 + D}{A + B/Z_0 + C Z_0 + D} = \frac{-1 + j\sqrt{2} - j\sqrt{2} - 1}{1 + j\sqrt{2} + j\sqrt{2} - 1} = \frac{-2}{j2\sqrt{2}} = j\frac{\sqrt{2}}{2}$$

Odd mode:

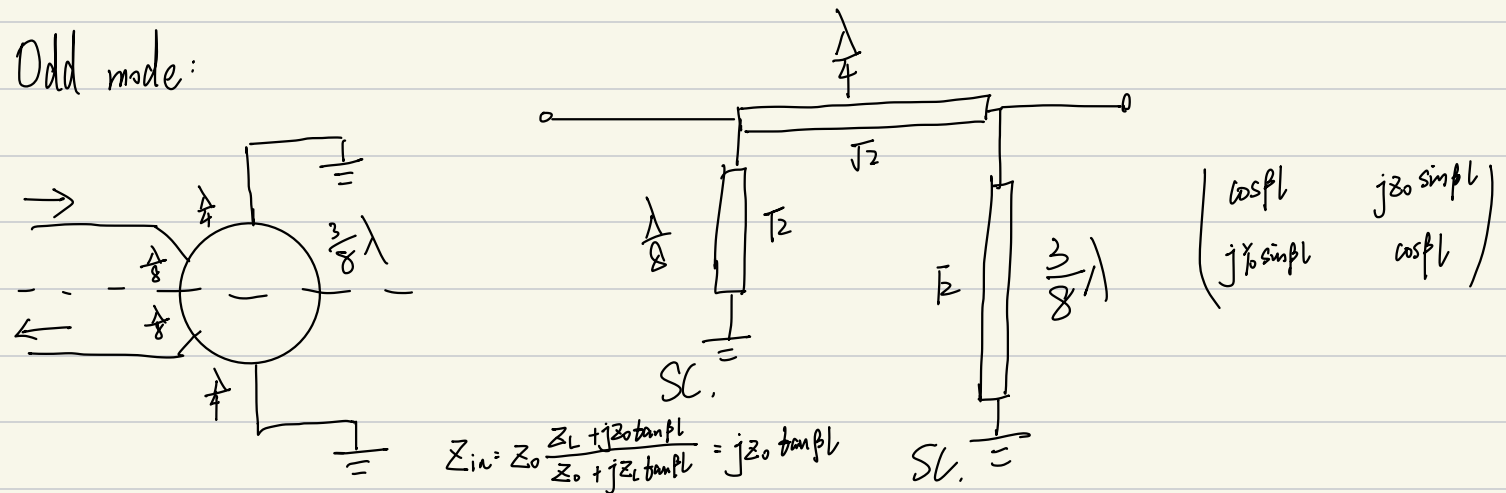

$$Z_{in} = Z_0 \cdot \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} = jZ_0 \tan \beta l$$

$$[ABCD]_{\text{odd}} = \begin{pmatrix} 1 & 0 \\ j\frac{Y_0}{2} & 1 \end{pmatrix} \begin{pmatrix} 0 & j\sqrt{2}Z_0 \\ j\frac{Y_0}{2} & 0 \end{pmatrix} \begin{pmatrix} 1 & 0 \\ j\frac{Y_0}{2} & 1 \end{pmatrix} = \begin{pmatrix} 0 & j\sqrt{2}Z_0 \\ j\frac{Y_0}{2} & 1 \end{pmatrix} \begin{pmatrix} 1 & 0 \\ j\frac{Y_0}{2} & 1 \end{pmatrix} = \begin{pmatrix} -1 & j\sqrt{2}Z_0 \\ j\sqrt{2}Y_0 & 1 \end{pmatrix}$$

$$S_{120} = \frac{2(AD - BC)}{A + B/Z_0 + Z_0 C + D} = \frac{2(-1 - 2)}{-1 + j\sqrt{2} + j\sqrt{2} - 1} = \frac{-6}{j2\sqrt{2}} = j \frac{3\sqrt{2}}{2}$$

$$S_{220} = \frac{-A + B/Z_0 - Z_0 C + D}{A + B/Z_0 + Z_0 C + D} = \frac{2}{j2\sqrt{2}} = -j \frac{\sqrt{2}}{2}$$

(b) Design a coupled line filter with fifth-order 3 dB equal ripple band-pass response, center frequency 2 GHz, bandwidth 200 MHz and impedance 50 Ω . Using a table, list down the low-pass prototype values, normalized inverter parameters, even and odd-mode characteristic impedances of the coupled line sections. Sketch the schematic diagram of the designed filter.

Answer: $N=5$ $\alpha_{max}=3\text{dB}$ Chebyshev bandpass filter $f_0=2\text{GHz}$ $BW=200\text{MHz}$ $Z_0=50\Omega$

5 3.4817 0.7618 4.5381 0.7618 3.4817 1.0000

$$\Delta = \frac{0.2}{2} = 0.1$$

n	g_n	$Z_0 J_n$	J_n	Z_{oe}	Z_{oo}
1	3.4817	0.2124	4.248×10^{-3}	62.88	41.64
2	0.7618	9.645×10^{-2}	1.929×10^{-3}	55.29	45.64
3	4.5381	8.448×10^{-2}	1.6896×10^{-3}	54.58	46.13
4	0.7618	8.448×10^{-2}	1.6896×10^{-3}	54.58	46.13
5	3.4817	9.645×10^{-2}	1.929×10^{-3}	55.29	45.64
6	1.0000	0.2124	4.248×10^{-3}	62.88	41.64

$$Z_0 J_1 = \sqrt{\frac{\pi \Delta}{2g_1 g_0}}$$

$$Z_0 J_n = \frac{\pi \Delta}{2\sqrt{g_n g_{n+1}}}$$

$$Z_0 J_{N+1} = \sqrt{\frac{\pi \Delta}{2g_N g_{N+1}}}$$

$$Z_{oe} = Z_0 [1 + Z_0 J_n + (Z_0 J_n)^2]$$

$$Z_{oo} = Z_0 [1 - Z_0 J_n + (Z_0 J_n)^2]$$

